



J1 and J2 should be connected to computer's that communicate. J3 then can eavesdrop depending on the position of the switch. When the switch is on the right, the transmission from J2 is intercepted; on the left - the transmission on the right. One does not need 3 computers; only 3 serial ports!